


VLSI - Assignment 2

Soham Vaishnav

2022112002

Q1.

(a) NOT

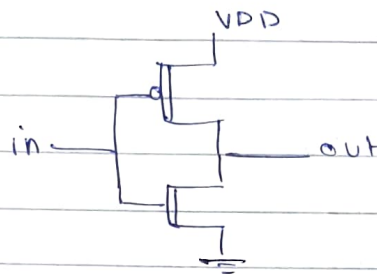

$$\text{max delay} = 5.08499 \times 10^{-11} \text{ s.}$$


(b) 5-input - AND

(c) 4-input - OR

(d) 2-input - XOR

plots &
delays attached
in pictures
after this
page.

Q2. 3-Not-gate Ring Osc \rightarrow

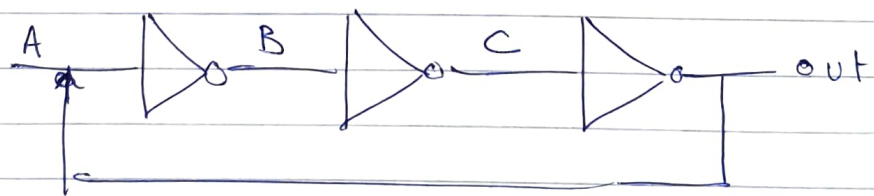

~~A~~ out follows ~~A~~ is complement of $A(t)$

$$\& A(t+1) = \text{out}$$

$$B(t) = A'(t)$$

$$\& C(t) = B'(t) = A(t).$$

$$\& \text{out}(t) = A'(t).$$

flow of
bits.



No. of Data Rows : 385

Measurements for Transient Analysis

trise	=	3.869565e-11	targ=	8.869565e-11	trig=	5.000000e-11
tfall	=	6.300415e-11	targ=	1.021300e-08	trig=	1.015000e-08
tpd	=	5.08499e-11				

ngspice 5 ->

Initial Transient Solution

Node	Voltage
a	0
b	0
c	0
d	0
e	0
vdd	1.8
out	8.4831e-09
vdd#branch	-1.78588e-11
ve#branch	0
vd#branch	0
vc#branch	0
vb#branch	0
va#branch	0

No. of Data Rows : 731

Measurements for Transient Analysis

trisea	=	2.761446e-10	targ=	3.261446e-10	trig=	5.000000e-11
tfalla	=	1.739981e-10	targ=	1.032400e-08	trig=	1.015000e-08
tpd	=	2.25071e-10				
triseb	=	2.761446e-10	targ=	3.261446e-10	trig=	5.000000e-11
tfallb	=	1.027400e-08	targ=	1.032400e-08	trig=	5.000000e-11
tpd	=	5.27507e-09				
trisee	=	2.761446e-10	targ=	3.261446e-10	trig=	5.000000e-11
tfallc	=	1.027400e-08	targ=	1.032400e-08	trig=	5.000000e-11
tpd	=	5.27507e-09				
trised	=	2.761446e-10	targ=	3.261446e-10	trig=	5.000000e-11
tfalld	=	1.027400e-08	targ=	1.032400e-08	trig=	5.000000e-11
tpd	=	5.27507e-09				
trisee	=	2.761446e-10	targ=	3.261446e-10	trig=	5.000000e-11
tfalle	=	1.027400e-08	targ=	1.032400e-08	trig=	5.000000e-11
tpd	=	5.27507e-09				

ngspice 5 ->

5_input_AND_mag.cir

-- ready --

Stop

Quit

01
(b)

c -> out

Circuit: * spice3 file created from 4_input.ext - technology: scmos

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Checking parameters for BSIM 3.2 model cmosp

Warning: Pd = 0 is less than V.

Warning: Ps = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosn

Warning: Pd = 0 is less than V.

Warning: Ps = 0 is less than V.

Initial Transient Solution

Node	Voltage
a	0
b	0
c	0
d	0
vdd	1.8
out	1.49449e-08
vdd#branch	-3.93867e-11
vd#branch	0
vc#branch	0
vb#branch	0
va#branch	0

No. of Data Rows : 370

Measurements for Transient Analysis

trisea	=	9.220763e-11	targ=	1.422076e-10	trig=	5.000000e-11
tfalla	=	1.406528e-07	targ=	1.508028e-07	trig=	1.015000e-08
tpd	=	7.03725e-08				
triseb	=	9.220763e-11	targ=	1.422076e-10	trig=	5.000000e-11
tfallb	=	1.507528e-07	targ=	1.508028e-07	trig=	5.000000e-11
tpd	=	7.54225e-08				
trisee	=	9.220763e-11	targ=	1.422076e-10	trig=	5.000000e-11
tfalle	=	1.507528e-07	targ=	1.508028e-07	trig=	5.000000e-11
tpd	=	7.54225e-08				
trised	=	9.220763e-11	targ=	1.422076e-10	trig=	5.000000e-11
tfalld	=	1.507528e-07	targ=	1.508028e-07	trig=	5.000000e-11
tpd	=	7.54225e-08				

ngspice 6 ->


4_input_OR_mag.cir

-- ready --

Stop

Quit

OT
(c)

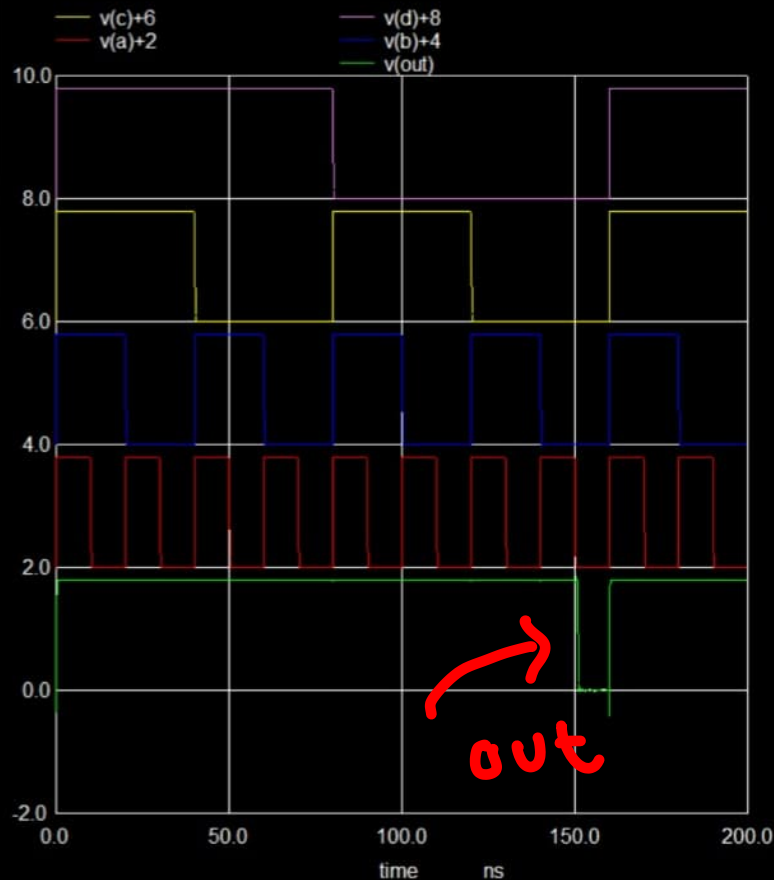

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Checking parameters for BSIM 3.2 model cmosn
Warning: Ps = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosn
Warning: Ps = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosn
Warning: Pd = 0 is less than V.
Warning: Ps = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosp
Warning: Pd = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosp
Warning: Pd = 0 is less than V.
Warning: Ps = 0 is less than V.

Checking parameters for BSIM 3.2 model cmosp
Warning: Pd = 0 is less than V.
Warning: Ps = 0 is less than V.

Initial Transient Solution

Node	Voltage
a	0
b	0
vdd	1.8
out	2.26166e-08
vdd#branch	-9.93418e-11
vb#branch	0
va#branch	0

No. of Data Rows : 318

Measurements for Transient Analysis

trisea	=	1.100765e-08	targ=	1.105765e-08	trig=	5.000000e-11
tfalla	=	3.097587e-08	targ=	3.102587e-08	trig=	5.000000e-11
tpd	=	2.09918e-08				
triseb	=	1.100765e-08	targ=	1.105765e-08	trig=	5.000000e-11
tfallb	=	3.097587e-08	targ=	3.102587e-08	trig=	5.000000e-11
tpd	=	2.09918e-08				

ngspice 8 ->


XOR_mag.cir

-- ready --

Stop

Quit

or
(d)

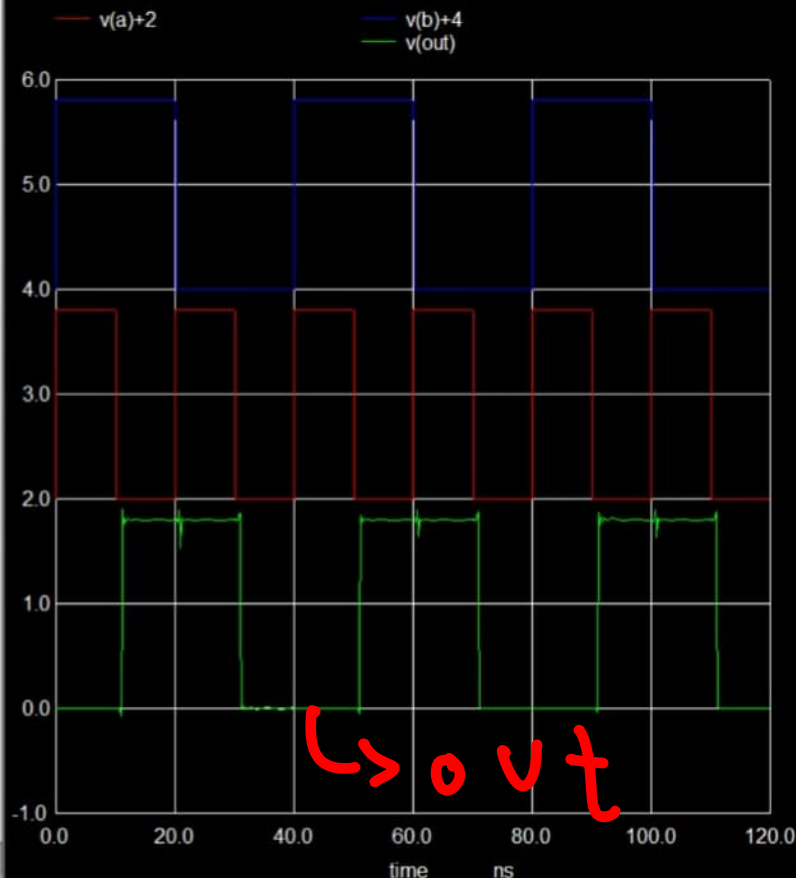

The plots for ngspice & magic simulaⁿ have been attached after this page.

No, the Function of 1 NOT-gate osc. will be the same in terms of input/output

but the periodicity of oscillation increases in case of 3-NOT gate osc due to added delay of 3 NOT gates. It is 3 times (nearly) less in 1-NOT gate osc.

⇒ less oscillations for 3-inverter osc.
than 1-inverter osc for same time frame.

Q3. Truth table

A ₂	A ₁	A ₀	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

} majority fⁿ


$$\therefore Y = (A_2')(A_1')(A_0) + (A_2)(A_1')(A_0) + (A_2)(A_1)(A_0)'$$

$$\therefore Y = (A_2')(A_1') \cdot 0 + (A_2)(A_1)(A_0) + (A_0) [(A_1)(A_2) + (A_1')(A_2)'] + (A_2)(A_1) \cdot 1$$

02

v(out)

magic

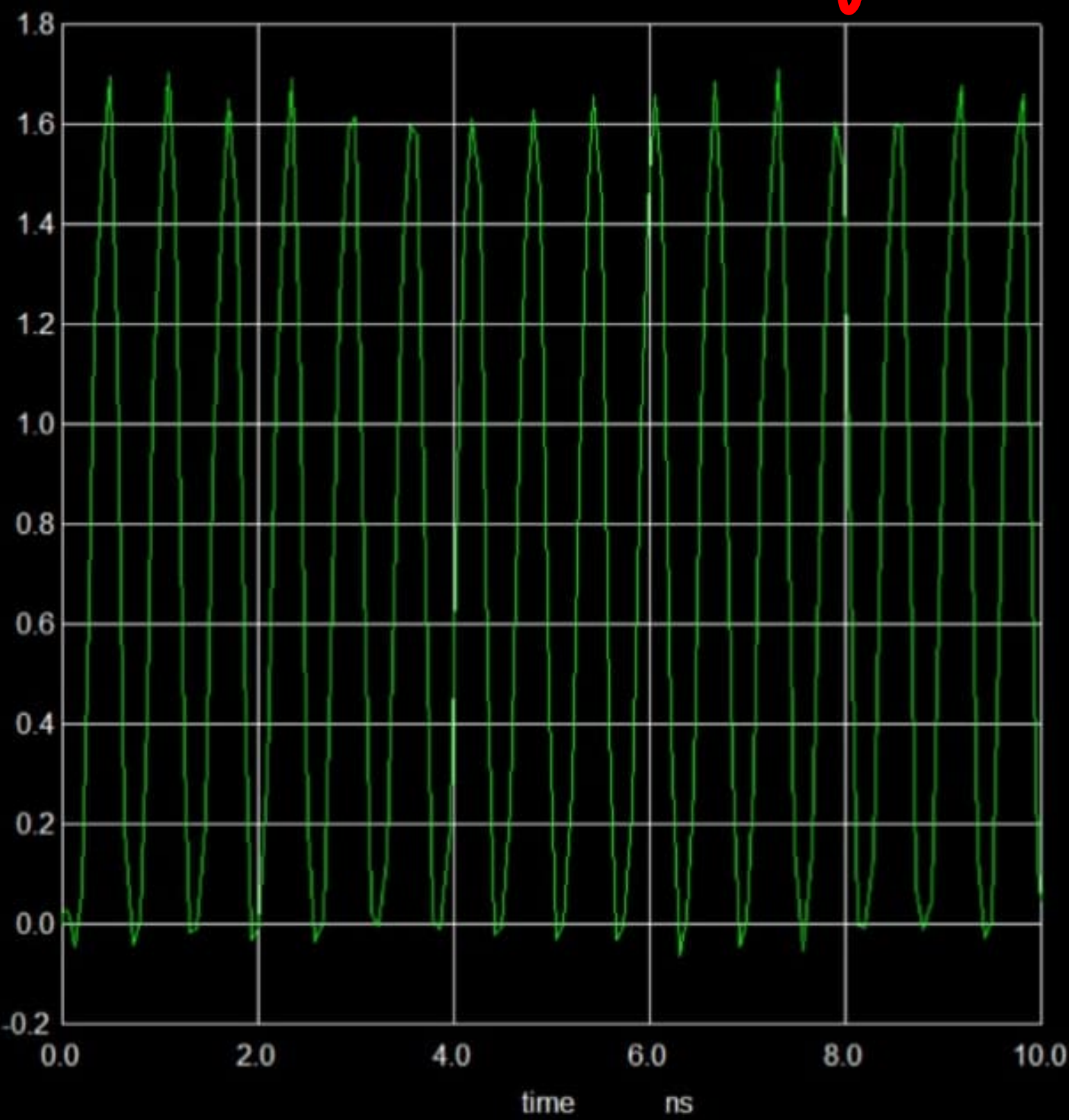


V


 σ

— v(w2)

ngspice

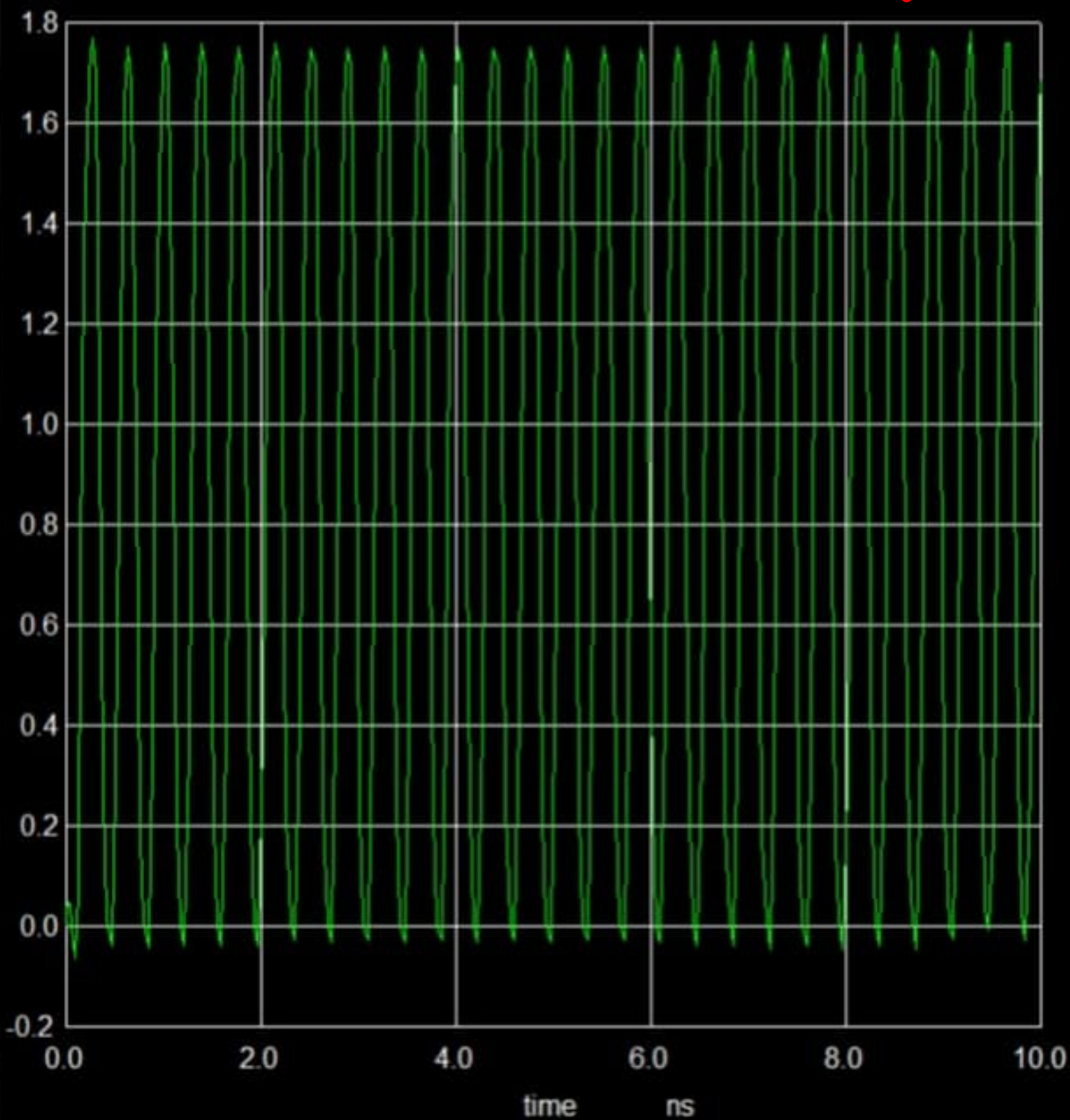

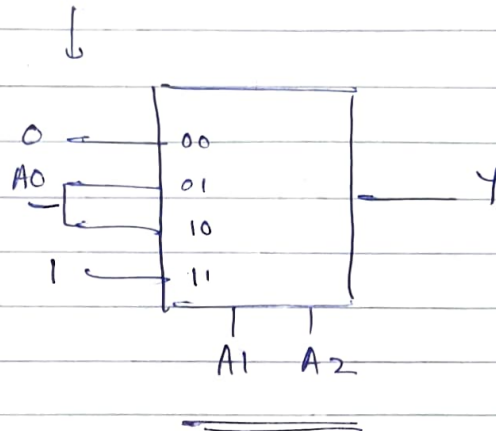These four terms in Y depict the function of a 4×1 MUX where A_2 & A_1 are select lines



Trend in delay : \rightarrow delay increases with temperature because the current flowing through CMOS decreases due to increase in V_{th}

\Rightarrow cap charges slowly so delay \uparrow .

Output pics attached after this page.


Q4 we need a circuit that gives absolute value of a number (3 bit — 4th bit signed)

logic : if A_3 (4th bit) = 0

then $S_2 = A_2$, $S_1 = A_1$ & $S_0 = A_0$


if $A_3 = 1$

then	$ \begin{array}{r} A_2' \quad A_1' \quad A_0' \\ + \quad 0 \quad 0 \quad 1 \\ \hline S_2 \quad S_1 \quad S_0 \end{array} $
------	---

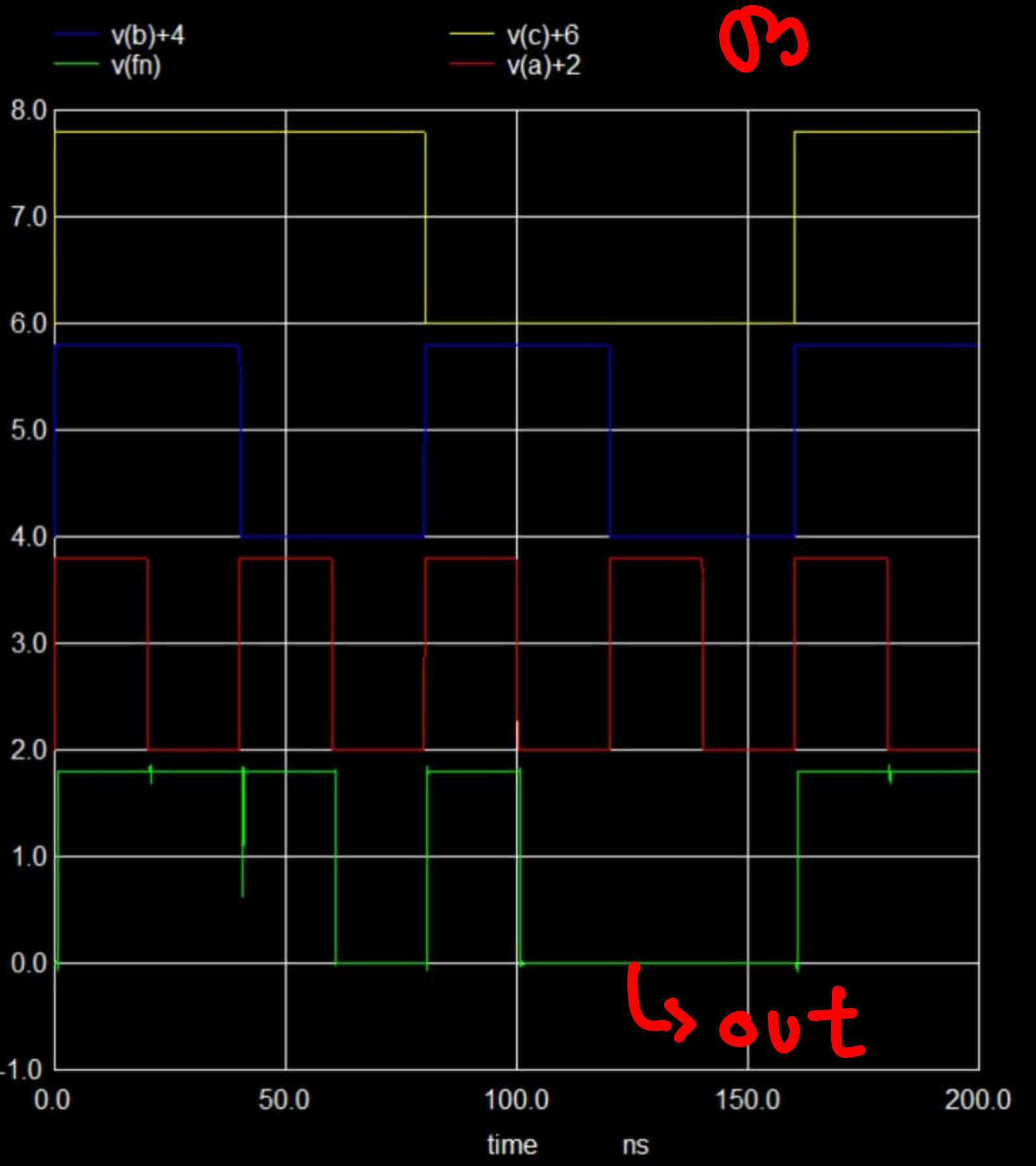

to get $A_2', A_1' \& A_0'$ we XOR them with A_3

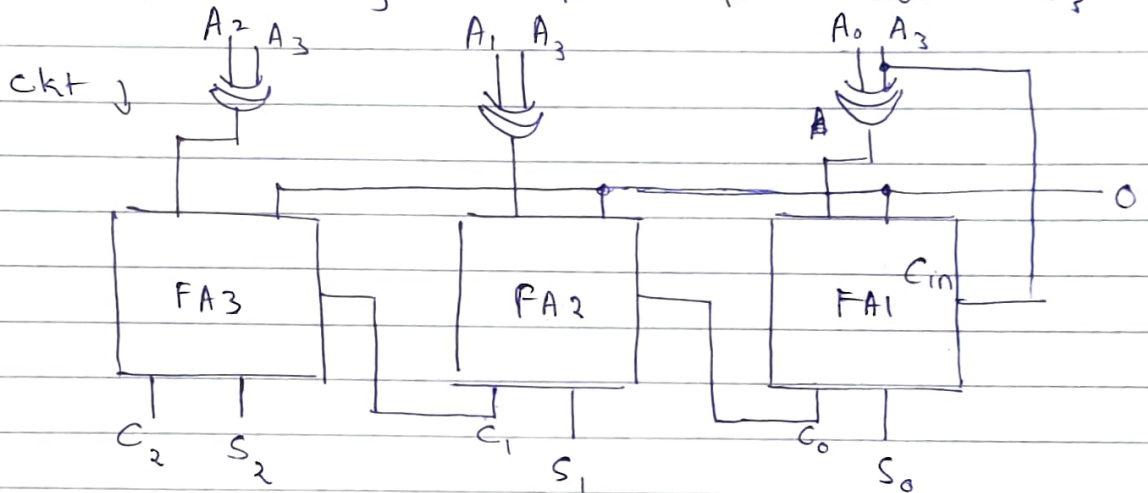Now first carry to first full adder = A_3



Output after this page.

Q5. As

(a) As temp \uparrow delays \uparrow because as V_{th} rises, the current reduces which essentially charges the capacitor more slowly thereby delaying the responses.

(b) delay trend as $C_L \uparrow$

delay \uparrow as $C_L \uparrow$ because $\tau = 0.67RC_L \uparrow$

C_L (fF)	delay (s)	C_L (fF)	delay (s)
2	6.74820×10^{-11}	12	9.1461×10^{-11}
4	7.22902×10^{-11}	14	9.5913×10^{-11}
6	7.75434×10^{-11}	16	1.0072×10^{-10}
8	8.2567×10^{-11}	18	10.579×10^{-11}
10	8.7143×10^{-11}	20	11.067×10^{-11}

←
Picc
after
this
page.

